

More bits, circuits, adders (From the last class)

CS 2130: Computer Systems and Organization 1

Xinyao Yi Ph.D.
Assistant Professor

Announcements

- Quiz 2 out later today, due Sunday at 11:59pm
- Homework 1 due Monday
- Homework 2 available Monday

Adder

Can we use this in parallel to add multi-bit numbers?


What is missing?

Consider:


$$\begin{array}{r} 11 \\ +01 \\ \hline \end{array}$$

3-input Adder

Add 3 1-bit numbers: a , b , c

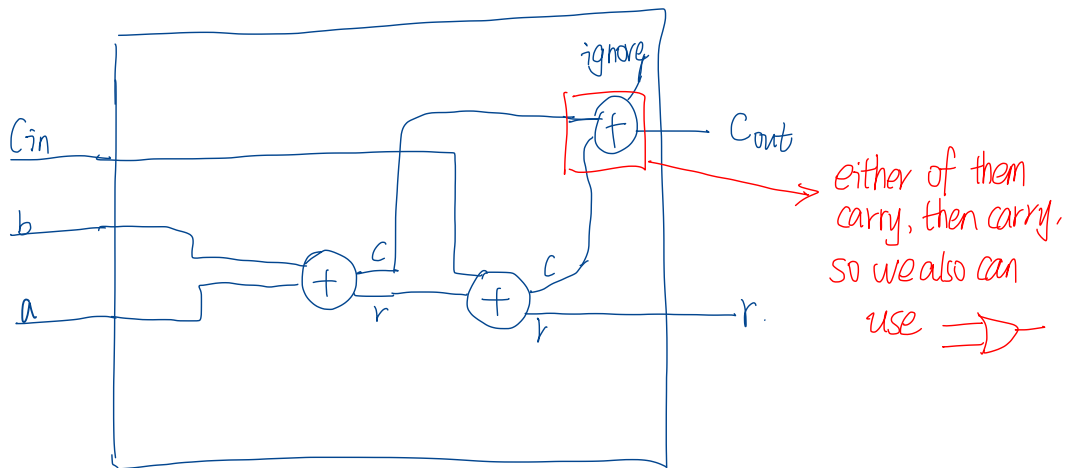


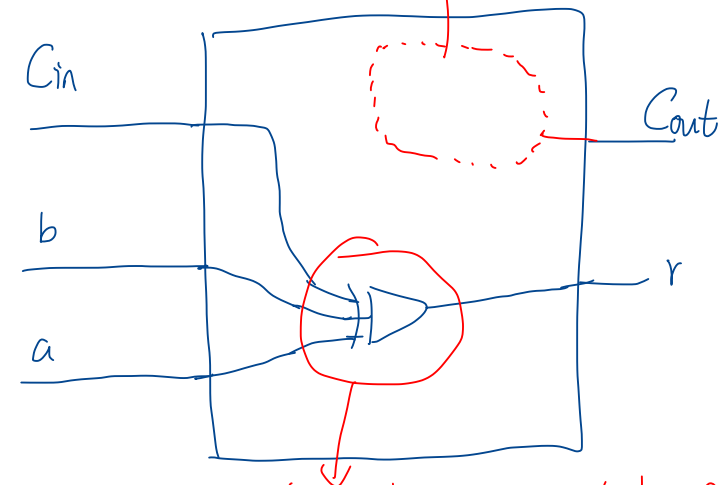for this part, you can think:
1 if and only if ≥ 2 .
Think about using and/or ?



2 ones $\Rightarrow$ even $\Rightarrow$ lowest bit is going to be 0
1 one and 2 zeros $\Rightarrow$ lowest bit: 1

Ripple-Carry Adder

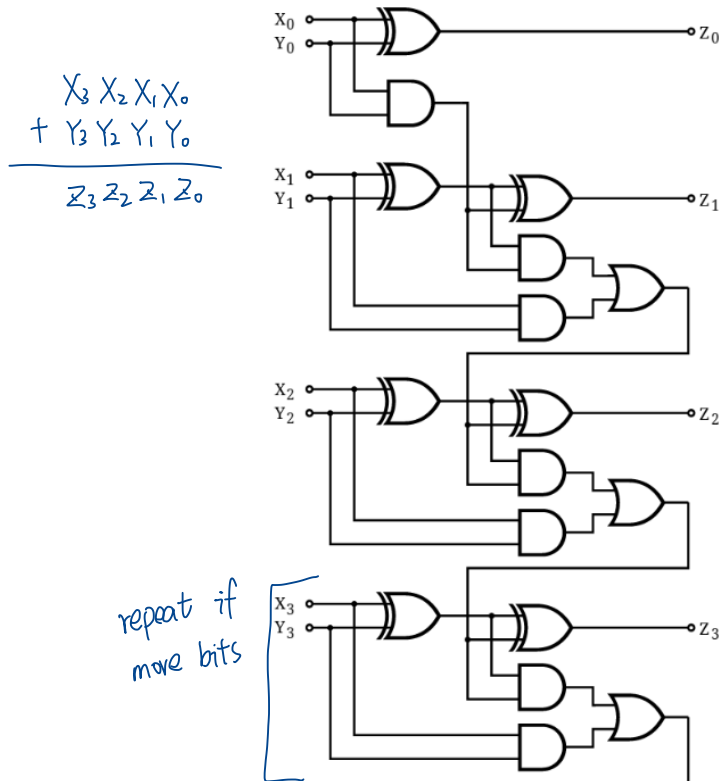

verify:

unsigned?

	1	1	1	1	(15)
+	1	1	1	1	(15)
drop	1	1	1	0	(14)

overflow!


signed?

	1	1	1	1	(-1)
+	1	1	1	1	(-1)
	1	1	1	0	(-2)


works!

Ripple-Carry Adder: Lowest-order Bit


(one bit 2 inputs adder)

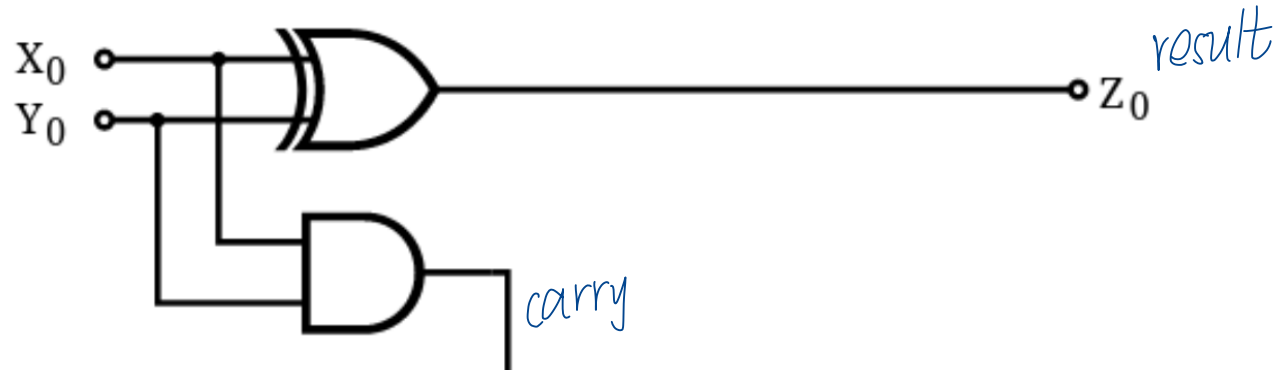

Ripple-Carry Adder: In General

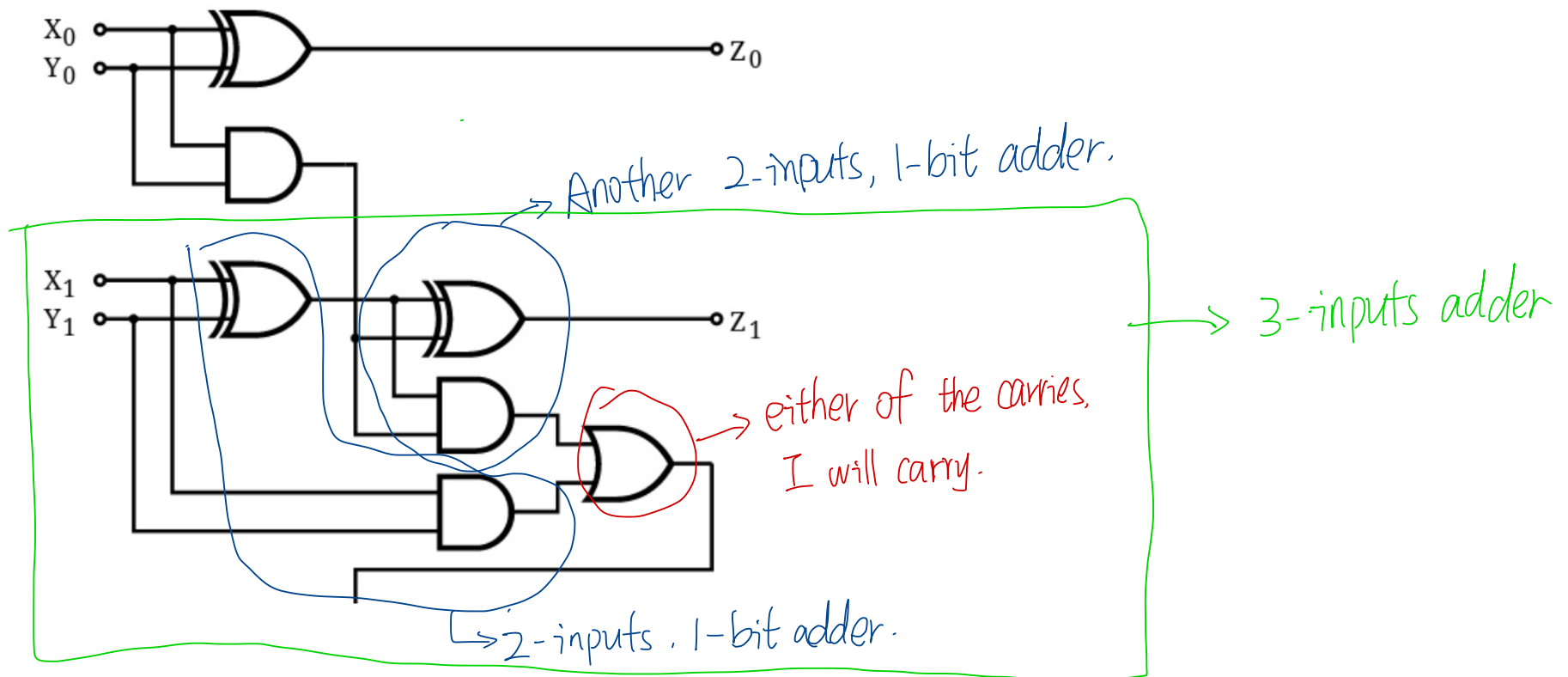

Ripple-Carry Adder: In General

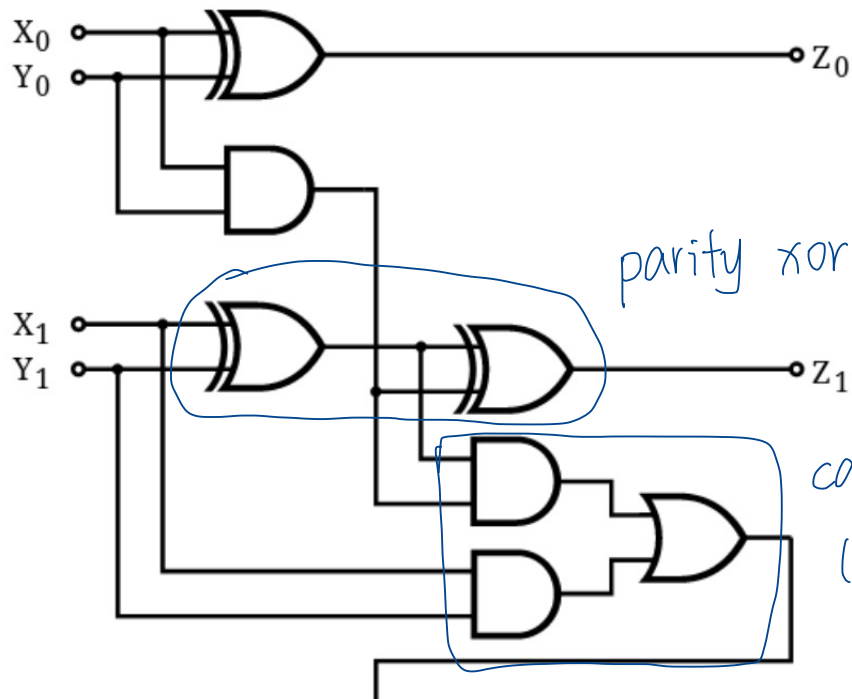


Clocks, Registers

CS 2130: Computer Systems and Organization 1

Xinyao Yi Ph.D.
Assistant Professor


What does this circuit do?

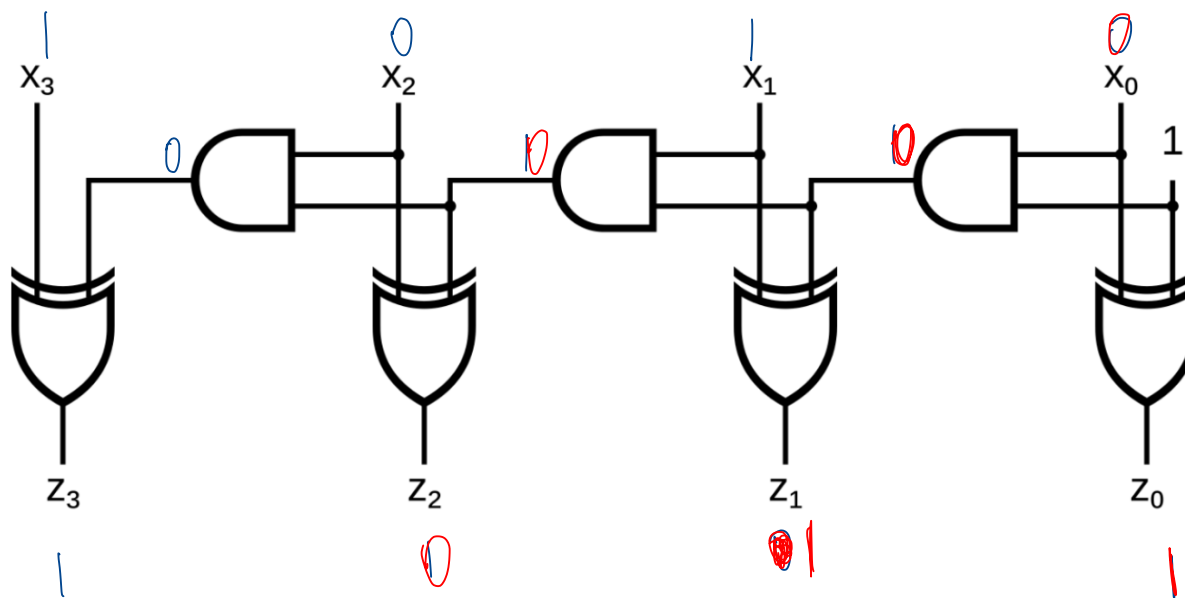


It add 1 !

Increment Circuit

I want a counter.

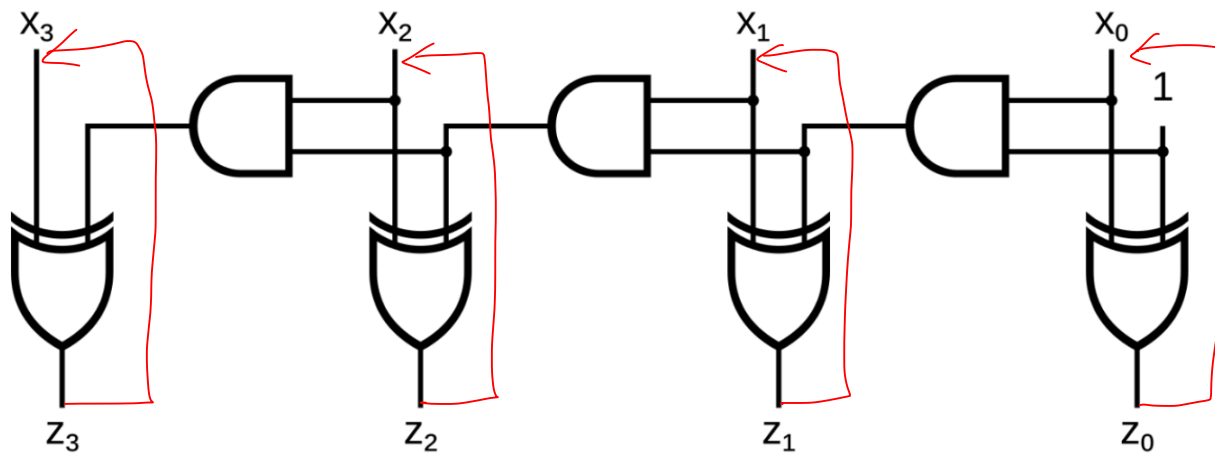

Idea:


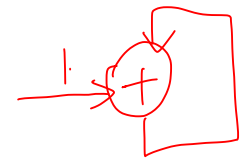


*output a one, then
feed itself back,
then I can count.*

glitch happens!


Gate Delay

What happens when I change my input?

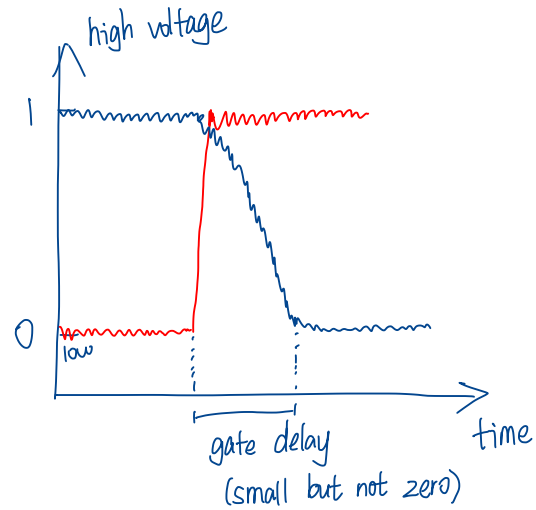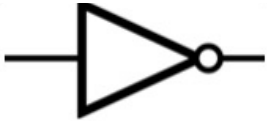


Building a Counter

So what we want to do:

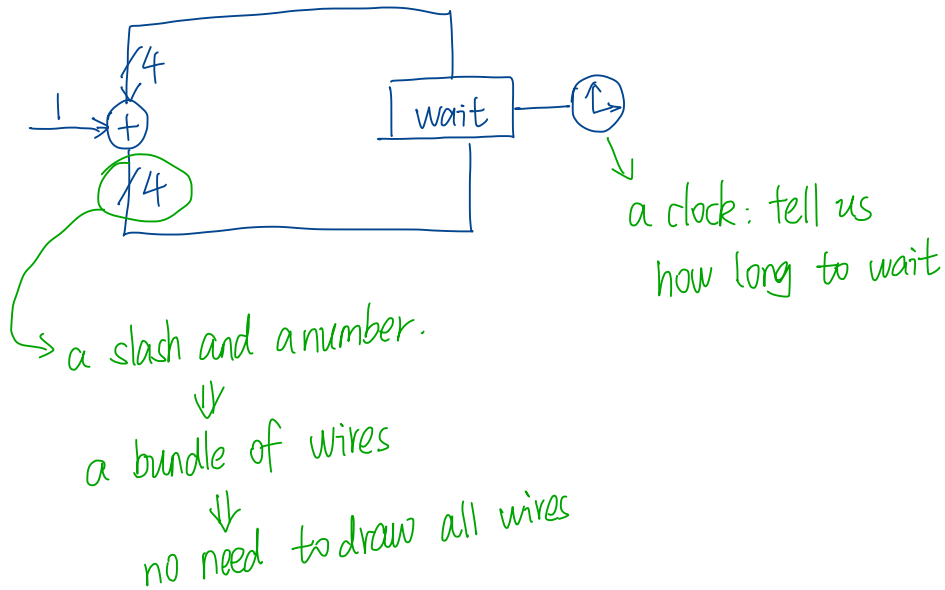


a register:

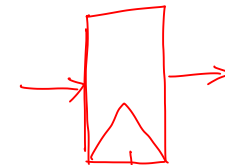

This triangle is the symbol of a clock.


1-bit Register Circuit

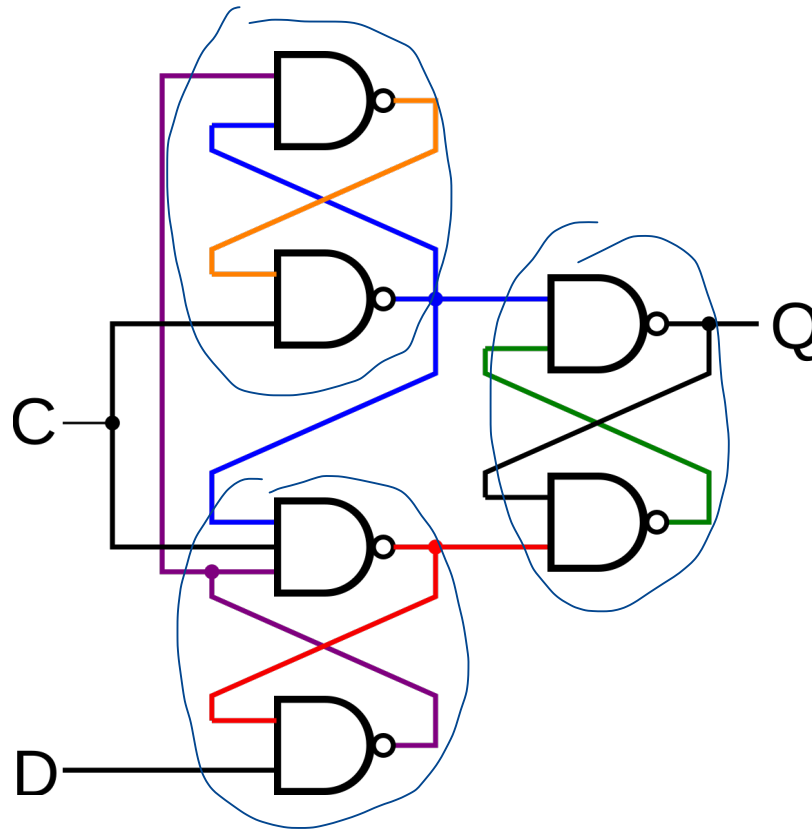


$\Rightarrow$ Do — NAND gate

0	0	1
0	1	1
1	0	1
1	1	0

1-bit Register Circuit

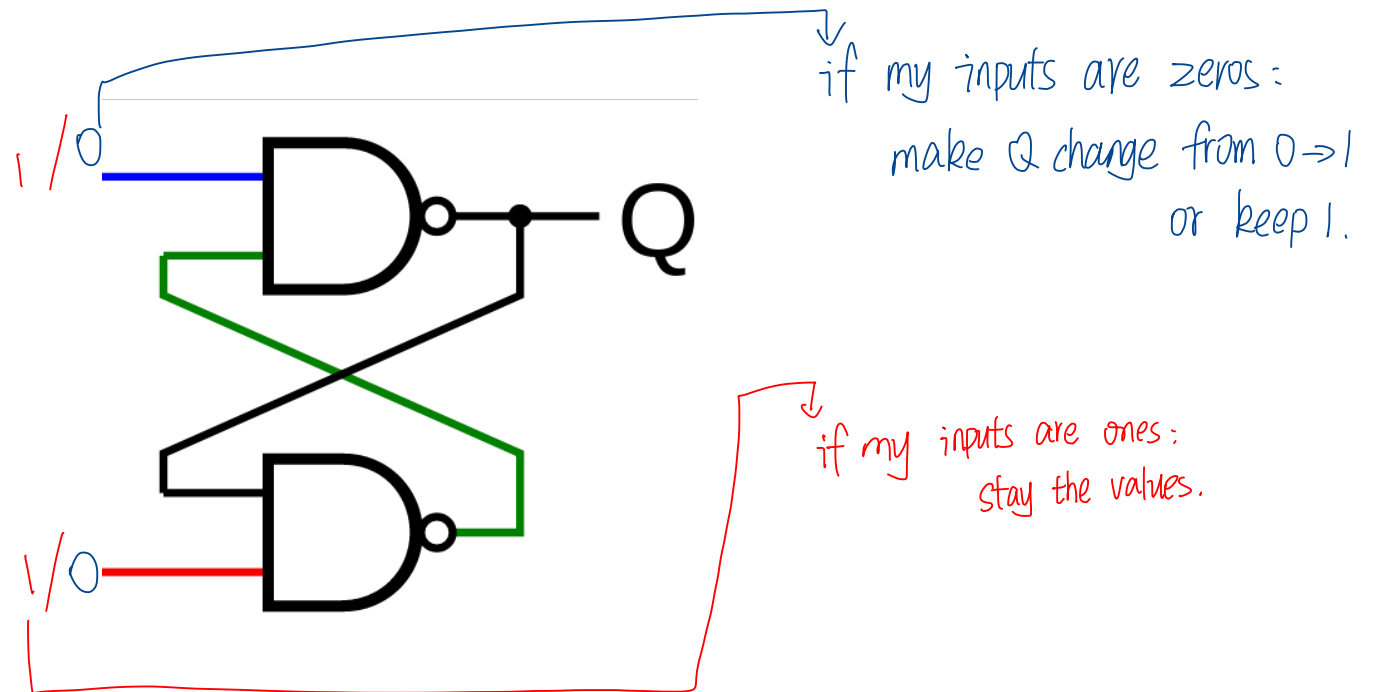

1-bit Register Circuit

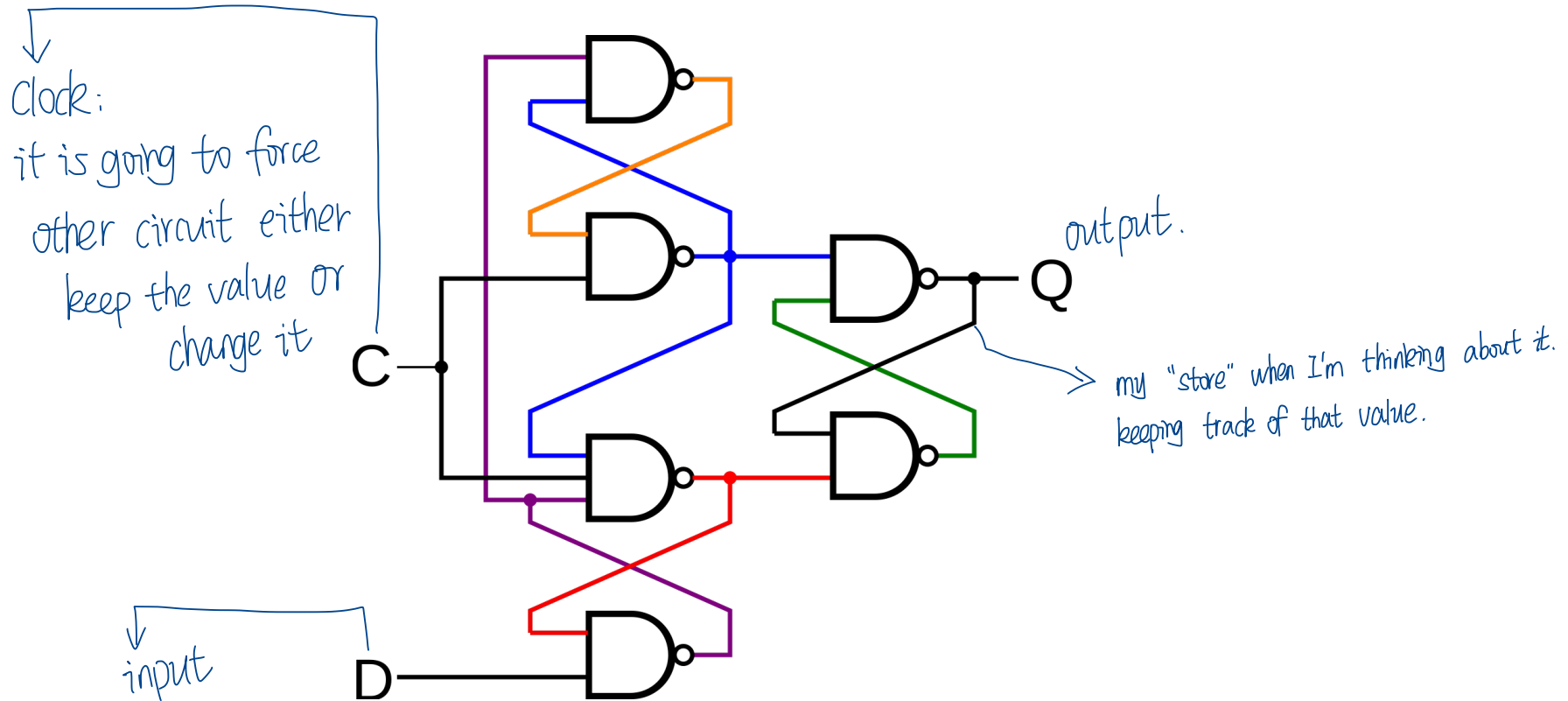


1-bit Register Circuit

When the clock is low:
The register monitors the input D, but it does not immediately update Q.


On the rising edge of the clock:
The register samples the value of D and immediately updates Q.

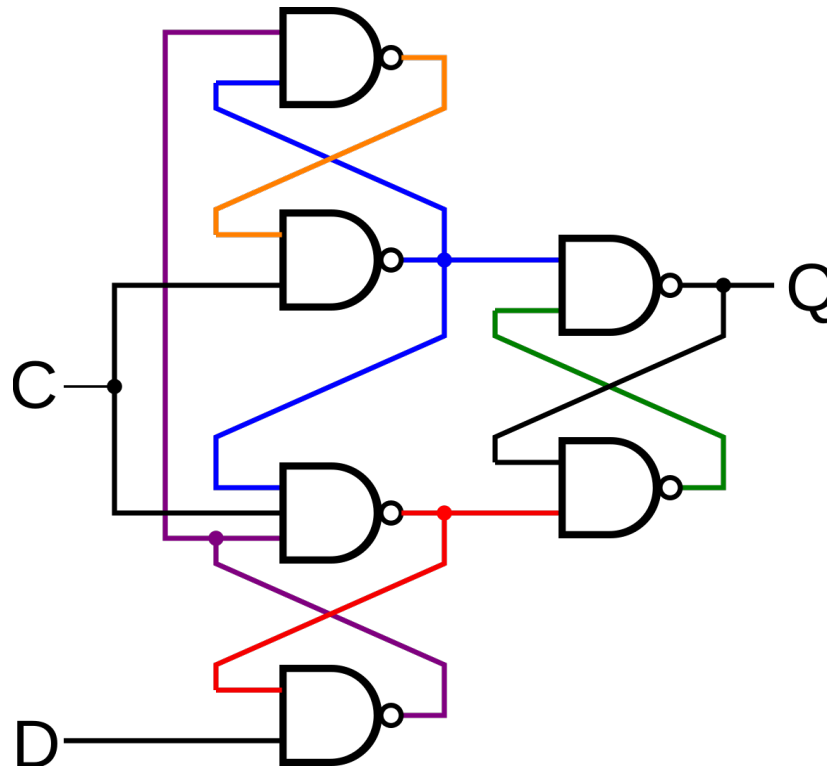At all other times: Even if D changes rapidly, Q remains unchanged until the next rising edge.



Building a Counter

four-bit register:

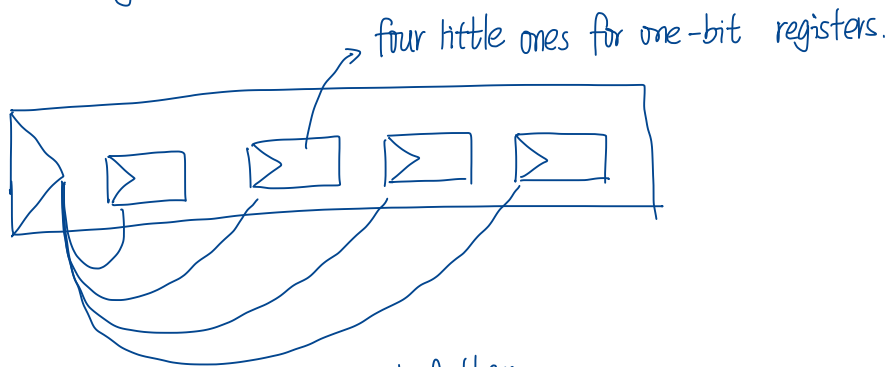

attach the clock to all of them.
they all have the same clock.